

## University of British Columbia Electrical and Computer Engineering Electrical and Biomedical Engineering Design Studio ELEC291/ELEC292

## Adding WAV Sound to the MSP430G2553

Copyright © 2021, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

The diagram below shows the connections required to add WAV sound to the MSP430G2553 using PWM. Please note that the 32.768kHz crystal has been removed. Also note that pin 7 is connected to both the BO230XS board and the 25Q32 flash memory.



